

**BITS-Pilani Dubai Campus**  
**I Sem 2021-22**  
**Digital Design Laboratory / ECE/INSTR/CS F215**  
**Submission Report**  
**Experiment No.- 9 (Sequence Detector and Shift Register)**

Name Anurag Kumar Jha

ID Number 2020A7PS0128U

**Hardware runs**

**Run 1: Parallel-in parallel-out**

**Truth Table**

S0=1, S1=1,

Input	Clk	Output
A B C D		QAQBQCQD
0000	1	0000
1010	1	1010
1111	1	1111

**Run 2: Serial-in Parallel-out (Right Shift)**

First load the '0000' to the O/P, with help of Parallel Load.

**Truth Table**

S0=1, S1=0,

Shift Right (I/P) Pin No.-2	No. of Pulses(n)	QAQBQCQD
1	1	1000
1	2	1100
1	3	1110
1	4	1111
0	5	0111
0	6	0011
0	7	0001
0	8	0000
1	9	1000

## Experiment No.- 9 (Sequence Detector and Shift Register)

Name Anurag Kumar Jha

ID Number 2020A7PS0128U

### Run 3: Serial-in Parallel-out (Left Shift)

First load the '0000' to the O/P, with help of Parallel Load.

#### Truth Table

S0=0, S1=1,

Shift Left (I/P) Pin No.-7	No. of Pulses(n)	Q <sub>A</sub> Q <sub>B</sub> Q <sub>C</sub> Q <sub>D</sub>
1	1	0001
1	2	0011
1	3	0111
1	4	1111
0	5	1110
0	6	1100
0	7	1000
0	8	0000
1	9	0001

#### Software runs

##### Run 4:

Sequence detector for '110': Write the Verilog code and testbench for the sequence detector as Moore machine.

```
module detector_110 (input x, clk, rst, output reg z);
parameter [1:0] S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
reg [1:0] present_state;
always @ (posedge clk, posedge rst) begin
z <= (present_state == S3) ? 1 : 0;
if (rst) begin
z <= 1'b0;
present_state <= S0;
end
else begin
case (present_state)
```

## Experiment No.- 9 (Sequence Detector and Shift Register)

**Name Anurag Kumar Jha**

**ID Number 2020A7PS0128U**

```
S0: begin
if (x) present_state <= #1 S1;
else present_state <= #1 S0;
end
S1: begin
if (x) present_state <= #1 S2;
else present_state <= #1 S0;
end
S2: begin
if (x) present_state <= #1 S2;
else present_state <= #1 S3;
end
S3: begin
if (x) present_state <= #1 S1;
else present_state <= #1 S0;
end
endcase
end // end of else begin
z<= (present_state == S3) ? 1 : 0;
end // end of always begin
endmodule
module t_exp9a;
wire z;
reg x,clk, rst;
initial #200 $finish;
initial begin clk = 0; forever #5 clk = ~clk; end
initial begin
x = 0; rst = 1;
#10 x=1;
```

## Experiment No.- 9 (Sequence Detector and Shift Register)

Name Anurag Kumar Jha

ID Number 2020A7PS0128U

```
#10 x= 0; rst =0;
```

```
#10 x= 1;
```

```
#10 x= 1;
```

```
#10 x= 0;
```

```
#10 x= 1;
```

```
#10 x= 0;
```

```
#10 x= 1;
```

```
#10 x= 0;
```

```
#10 x= 1;
```

```
#10 x= 1;
```

```
#10 x= 0;
```

```
#10 x= 0;
```

```
#10 x= 0;
```

```
#10 x= 1;
```

```
#10 x= 0;
```

```
#10 x= 1;
```


```
end
```

```
detector_110 u(x,clk,rst,z);
```

```
endmodule
```

**Q:** Paste the Image of your **Simvision** window where you get the waveforms for the above code.

**A:**

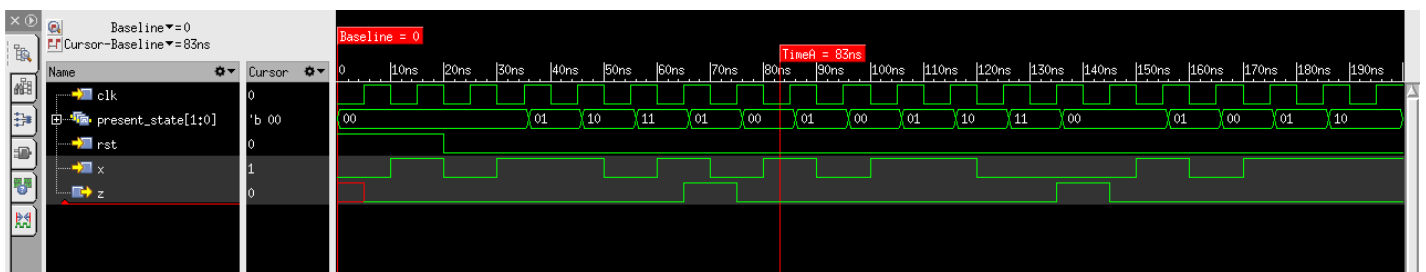

## Experiment No.- 9 (Sequence Detector and Shift Register)

Name Anurag Kumar Jha

ID Number 2020A7PS0128U

Q. Complete the state table below from the waveform observed.

### State Table

Present state		Next state	Output
state [1:0]	x_in	next_state [1:0]	y_out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	11	0
10	1	10	0
11	0	00	1
11	1	01	1

### Run 5:

4-bit universal shift register: Write Verilog code and testbench for 4-bit universal shift register.

```
module uni_shift_reg (input shift_L, shift_R, clk, input [3:0] parallel_in, input [1:0] mode, output reg [3:0] parallel_out);
```

```
always @ (negedge clk) begin
```

```
case (mode)
```

```
0: parallel_out <= parallel_out; // for mode 0 data retain as it is
```

```
1: parallel_out <= {parallel_out [2:0], shift_L}; // for mode 1 shift left
```

```
2: parallel_out <= {shift_R, parallel_out [3:1] }; // for mode 2 shift right
```

```
3: parallel_out <= parallel_in; // for mode 3 parallel data in
```

```
default: parallel_out <= 4'b0;
```

```
endcase
```

```
end
```

```
endmodule
```

```
// Test Bench
```

```
module tb;
```

```
reg shift_L, shift_R, clk;
```

## Experiment No.- 9 (Sequence Detector and Shift Register)


Name Anurag Kumar Jha

ID Number 2020A7PS0128U

```
reg [1:0] mode;
reg [3:0] parallel_in;
wire [3:0] parallel_out;
initial
begin
clk = 1#39;b0;
repeat (300) # 5 clk = ~clk; // clock is of time period 10 and 50% duty cycle.
end
initial
begin
#00 mode = 2#39;b11; parallel_in=4#39;b0000; shift_L=1; shift_R=1;
#40 mode =2#39;b01; shift_L=1;shift_R=0;parallel_in =4#39;b0000;
#40 mode =2#39;b11; parallel_in=4#39;b0000;
#40 mode =2#39;b10; shift_R=1;shift_L=0;
#40 mode =2#39;b10; shift_R=0;shift_L=1;
#40 mode =2#39;b11; parallel_in =4#39;b1010;
#40 mode =2#39;b00; parallel_in =4#39;b0000;
#40 $stop;
end
uni_shift_reg u(shift_L, shift_R, clk, parallel_in,mode, parallel_out);
endmodule
```

**Q:** Paste the Image of your **Simvision** window where you get the waveforms for the above code.

**A:**

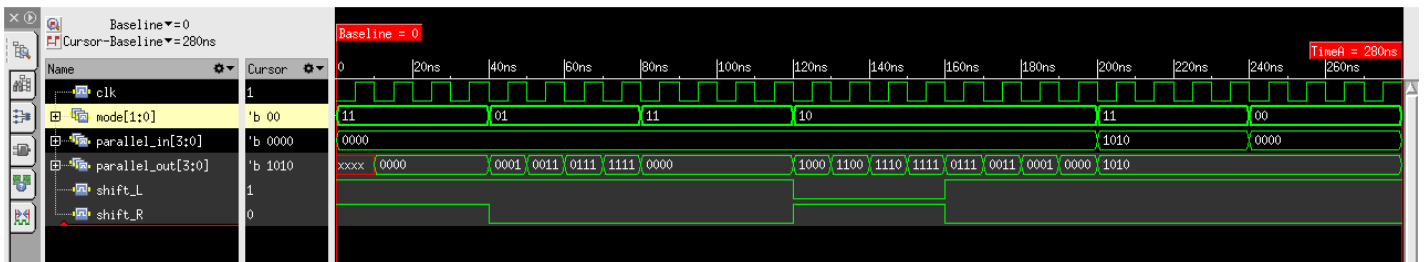

## Experiment No.- 9 (Sequence Detector and Shift Register)

Name Anurag Kumar Jha

ID Number 2020A7PS0128U

Q. Complete the truth table below from the waveform observed

Truth Table

Mode	No. of Clk Pulses (n)	Parallel I/P	Shift L (I/P)	Shift R (I/P)	Parallel O/P
11	1	0000	1	1	0000
11	2	0000	1	1	0000
11	3	0000	1	1	0000
11	4	0000	1	1	0000
01	5	0000	1	0	0001
01	6	0000	1	0	0011
01	7	0000	1	0	0111
01	8	0000	1	0	1111
11	9	0000	1	0	0000
11	10	0000	1	0	0000
11	11	0000	1	0	0000
11	12	0000	1	0	0000
10	13	0000	0	1	1000
10	14	0000	0	1	1100
10	15	0000	0	1	1110
10	16	0000	0	1	1111
10	17	0000	1	0	0111
10	18	0000	1	0	0011
10	19	0000	1	0	0001
10	20	0000	1	0	0000
11	21	1010	1	0	1010
11	22	1010	1	0	1010
11	23	1010	1	0	1010
11	24	1010	1	0	1010
00	25	0000	1	0	1010
00	26	0000	1	0	1010
00	27	0000	1	0	1010

**Assignment** All assignments are to be submitted strictly before start of next lab session through online only. Late assignments will not be entertained and will be awarded '0' marks.

1. Write the Verilog code and testbench for serial in serial out shift register.

Ans: Link1: <https://www.edaplayground.com/x/7bEe>

2. Write the Verilog code and testbench for serial in parallel out shift register.

## Experiment No.- 9 (Sequence Detector and Shift Register)

Name Anurag Kumar Jha

ID Number 2020A7PS0128U

Ans: Link2: <https://www.edaplayground.com/x/VCP6>

Self-Practice and self-evaluation (Very Important)

4-bit shift register: Below is the code for shift register using blocking statements. Write the testbench for the same and identify the issues when using blocking statements.

```
module shift_reg (output reg A, input E, clk, rst);
  reg B, C, D;
  always @ (posedge clk, posedge rst) begin
    if (rst == 1'b1) begin
      A=0;
      B = 0;
      C = 0;
      D = 0;
    end
    else begin
      A = B;
      B = C;
      C = D;
      D = E;
    end
  end
end
endmodule
```