

**BITS-Pilani Dubai Campus**  
**I Sem 2021-22**  
**Digital Design Laboratory / ECE/INSTR/CS F215**  
**Submission Report**  
**Experiment No.- 8 (Finite State Machines)**


Name Harsh Vegad

ID Number: 2020A7PS0152U

Hardware runs

Run 1:

Diagram

 

Q. Complete the state table by observing the outputs on LED panel.

Present state			Next state		Output
Q1(t)	Q0(t)	X	Q1(t+1)	Q0(t+1)	Z
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	0	0	0

## Experiment No.- 8 (Finite State Machines)

Name Harsh Vegad


ID Number: 2020A7PS0152U

1	1	1	0	1	0
---	---	---	---	---	---

### State Table

Q. Draw the State diagram from above state table?

Ans.

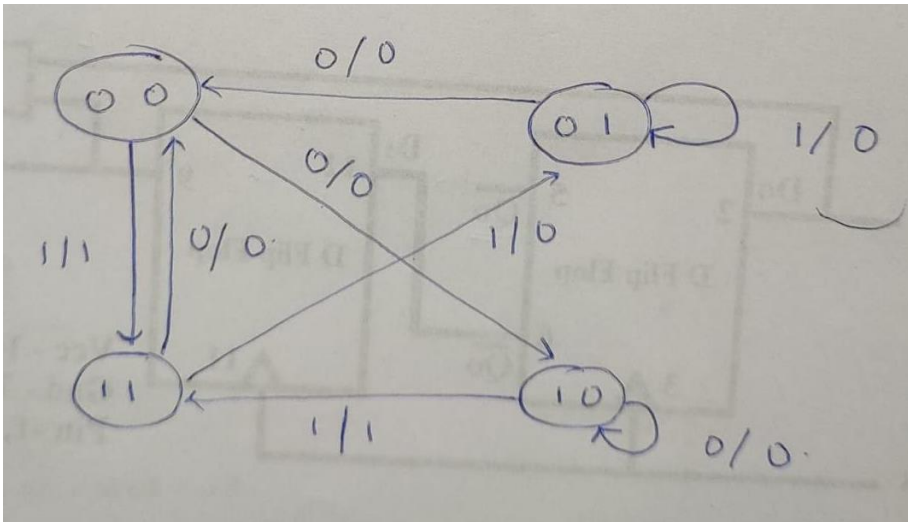

Q. Which types of Machine it is?


Ans. Mealy Machine. The output Z is dependent on Q1(present state) and X.

### Software runs

#### Run 2: Mealy Machine: Zero detector after series of 1

Q: Paste the Image of your **Simvision** window where you get the waveforms for the above code.

A:

 

## Experiment No.- 8 (Finite State Machines)

Name Harsh Vegad

ID Number: 2020A7PS0152U

Q. Complete the state table below from the waveform observed.


### State Table

Present state		Next state	Output
state [1:0]	t_x_in	next_state [1:0]	t_y_out
S0 (00)	0	00	0
S0 (00)	1	01	0
S1 (01)	0	00	1
S1 (01)	1	11	0
S2 (10)	0	00	1
S2 (10)	1	10	0
S3 (11)	0	00	1
S3 (11)	1	10	0

### Run 3: Moore Machine: Zero detector after series of 1

Q: Paste the Image of your **Simvision** window where you get the waveforms for the above code.

A:

 

Q. Complete the state table below from the waveform observed.

### State Table

Present state		Next state	Output
state [1:0]	t_x_in	next_state [1:0]	t_y_out
S0 (00)	0	00	0
S0 (00)	1	01	0
S1 (01)	0	00	1
S1 (01)	1	11	0
S2 (10)	0	00	1
S2 (10)	1	10	0
S3 (11)	0	00	1
S3 (11)	1	10	0

## Experiment No.- 8 (Finite State Machines)


Name Harsh Vegad

ID Number: 2020A7PS0152U

S0	0	S1	S0
S0	1	S1	S0
S1	0	S2	S1
S1	1	S2	S1
S2	0	S3	S2
S2	1	S3	S2
S3	0	S0	S3
S3	1	S0	S3

**Assignment** All assignments are to be submitted strictly before start of next lab session through online only. Late assignments will not be entertained and will be awarded '0' marks.

 1. Write a Verilog model of the Mealy FSM described by below the state diagram. Develop a test bench and demonstrate that the machine state transitions and output correspond to its state diagram.



Ans: Link1: <https://www.edaplayground.com/x/BvQu>

2. Draw the state diagram of the machine described by the Verilog model given below.

```
module Prob_1 ( output reg y_out, input x_in, clk, reset);
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10, s3 = 2'b11;
```

## **Experiment No.- 8 (Finite State Machines)**

**Name Harsh Vegad**

**ID Number: 2020A7PS0152U**

```
reg [1:0] state, next_state;
always @ ( posedge clk, negedge reset) begin
if (reset == 1'b0) state <= s0;
else
state <= next_state;
always @(state, x_in) begin
y_out = 0;
next_state = s0;
case (state)
s0: if x_in = 1 begin y_out = 0; if (x_in) next_state = s1; else next_state = s0; end
s1: if x_in = 1 begin y_out = 0; if (x_in) next_state = s2; else next_state = s1; end
s2: if x_in = 1 begin y_out = 1; if (x_in) next_state = s3; else next_state = s2; end
s3: if x_in = 1 begin y_out = 1; if (x_in) next_state = s0; else next_state = s3; end
default: next_state = s0;
endcase
end
endmodule
```


**Ans: Link2: <https://www.edaplayground.com/x/E5Wm>**

**State Diagram:**

## Experiment No.- 8 (Finite State Machines)

Name Harsh Vegad

ID Number: 2020A7PS0152U

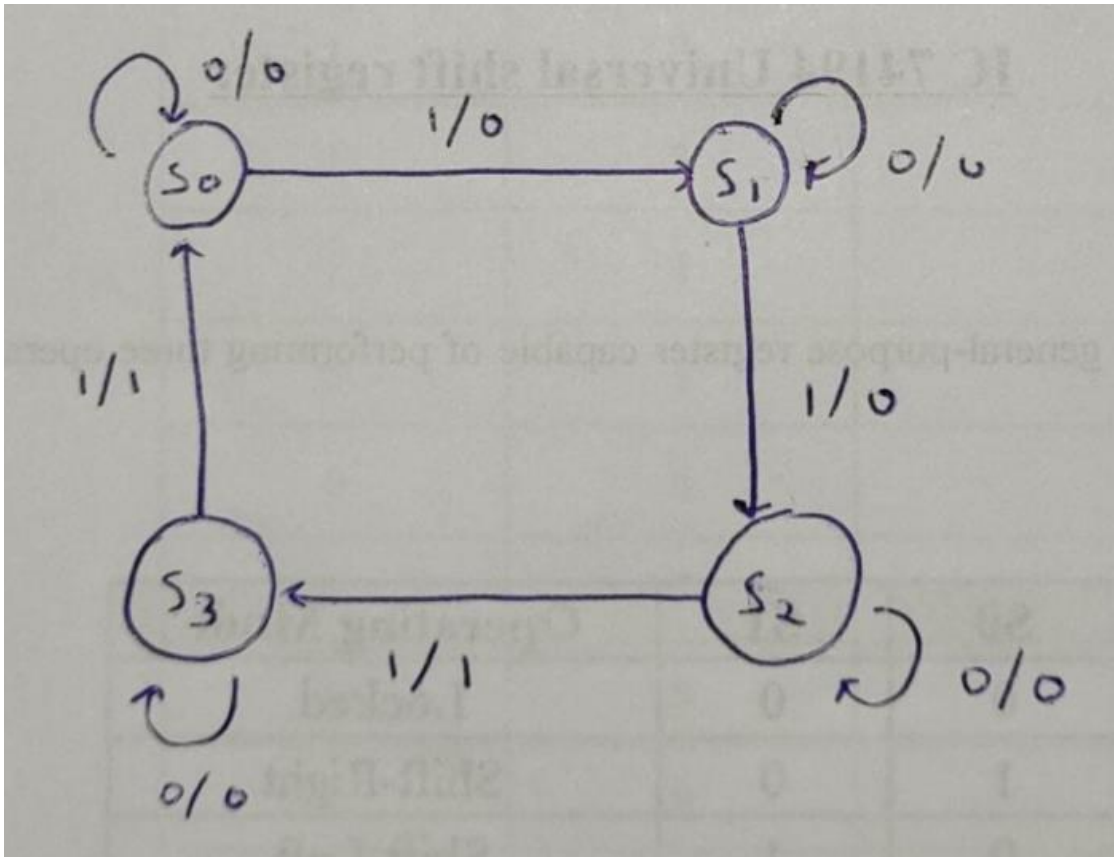


### Self-Practice and self-evaluation

1. Write a Verilog model of the Moore FSM described by the below state diagram. Develop a test bench and demonstrate that the machine's state transitions and output correspond to its state diagram.

## Experiment No.- 8 (Finite State Machines)

Name Harsh Vegad

ID Number: 2020A7PS0152U

 

2. Draw the state diagram of the machine described by the Verilog model given below.

```
module Prob_2 ( output reg y_out, input x_in, clk, reset);
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10, s3 = 2'b11;
reg [1:0] state, next_state;
always @ ( posedge clk, negedge reset) begin
if (reset == 1'b0) state <= s0;
else
state <= next_state;
always @(state, x_in) begin
y_out = 0;
next_state = s0;
case (state)
s0: if x_in = 1 begin y_out = 0; if (x_in) next_state = s1; else next_state = s0; end
s1: if x_in = 1 begin y_out = 0; if (x_in) next_state = s2; else next_state = s1; end
s2: if x_in = 1 if (x_in) begin next_state = s3; y_out = 0; else begin next_state = s2; y_out = 1; end
s3: if x_in = 1 begin y_out = 1; if (x_in) next_state = s0; else next_state = s3; end
default: next_state = s0;
endcase
end
endmodule
```